



Muxes

Presented By: Trevor Abel, Ryan Hinson,
Samuel Manos, and Mark Neitzel



Why Are Muxes Important?




- A multiplexer is a combinational circuit that has many data inputs and a single output that depends on control or select inputs.
- Muxes are mainly used to increase the amount of data that can be sent over the network within a certain amount of time and bandwidth.
- Multiplexers are used to select either a register operand (0) or a constant operand (1).



Instructions That Muxes Support

- A multiplexer is a logic gates circuit used to fetch a bit of data from memory at a given memory address. A processor has several multiplexers (MUX) controlling the data and address buses.
- Multiplexers are switches allowing the processor to select data from multiple data sources.
- To select which data source should be used a multiplexer has one or more control lines (a.k.a. Selectors).
- The output of a multiplexer is the selected data.

Overview aka how it do?

   

Test Cases

```
module MUXTEST();
    reg[4:0] A, B;
    reg S;
    reg clk;
    wire 0;

    MUX5 DUT(0, A, B, S);

    always
        #1 clk = ~clk;

    initial
    begin
        clk = 1'b0;
        A = 5'h00;
        B = 5'h00;
        S = 1'b0;

        @(negedge clk)
            A = 5'h00;
            B = 5'h00;
        @(negedge clk)
            A = 5'h0F;
            B = 5'h00;
        @(negedge clk)
            A = 5'h00;
            B = 5'h0F;
        @(negedge clk)
            A = 5'h10;
            B = 5'h00;
        @(negedge clk)
            A = 5'h00;
            B = 5'h10;
        @(negedge clk)
            A = 5'h1F;
            B = 5'h00;
```

```
        @(negedge clk)
            S = 1'b1;
            A = 5'h00;
            B = 5'h00;
        @(negedge clk)
            A = 5'h01;
            B = 5'h00;
        @(negedge clk)
            A = 5'h00;
            B = 5'h01;
        @(negedge clk)
            A = 5'h01;
            B = 5'h01;
        @(negedge clk)
            A = 5'h06;
            B = 5'h00;
        @(negedge clk)
            A = 5'h00;
            B = 5'h06;
        @(negedge clk)
            A = 5'h06;
            B = 5'h06;
        @(negedge clk)
            A = 5'h1A;
            B = 5'h00;
        @(negedge clk)
            A = 5'h00;
            B = 5'h1A;
        @(negedge clk)
            A = 5'h1A;
            B = 5'h1A;
        @(negedge clk)
            A = 5'h1F;
            B = 5'h00;
```

```
        @(negedge clk)
            $finish;
    end

    always @(A or B or S)
        #1 $display("At t=%T", $time, "|", "S=%b A=%b B=%b 0=%b", S, A, B, 0);

endmodule
```

```
module multiplexer_test();

    reg A, B, S;
    wire F;

    multiplexer DUT(A, B, S, F);

    initial
    begin
        A <= 0;
        B <= 0;
        S <= 0;
        #11
        $display("F = %d", F);
        A <= 0;
        B <= 0;
        S <= 1;
        #11
        $display("F = %d", F);
        A <= 0;
        B <= 1;
        S <= 0;
        #11
        $display("F = %d", F);
        A <= 0;
        B <= 1;
        S <= 1;
        #11
        $display("F = %d", F);
        A <= 1;
        B <= 0;
        S <= 0;
        #11
        $display("F = %d", F);
        A <= 1;
        B <= 1;
        S <= 0;
        #11
        $display("F = %d", F);
        A <= 1;
        B <= 1;
        S <= 1;
        #11
        $display("F = %d", F);
    end
```

```
        $display("F = %d", F);
        A <= 0;
        B <= 1;
        S <= 1;
        #11
        $display("F = %d", F);
        A <= 1;
        B <= 0;
        S <= 0;
        #11
        $display("F = %d", F);
        A <= 1;
        B <= 0;
        S <= 1;
        #11
        $display("F = %d", F);
        A <= 1;
        B <= 1;
        S <= 0;
        #11
        $display("F = %d", F);
        A <= 1;
        B <= 1;
        S <= 1;
        #11
        $display("F = %d", F);
    end
```

end

endmodule

Select	Inputs		Output
0	0	0	0
0	0	1	1
1	1	0	1
1	1	1	1




Issues with Muxes Implementations


- One of the most common implementation problems comes with moving a completed MUX into a full processor. When implementing a MUX into a full processor you can get an unexpected “x” value when it was working by itself.
- Another issue is mislabeling a variable and not listing it as a register then it will produce an output that tells you that the register you are trying to use does not exist.
- The other issues can either stem from misspelling or missing a line of code which would make your mux no longer work and integration into a single cycle processor impossible.

Gate Delay - 5 Bit Mux

Because of parallelism, muxes work all at the same time.

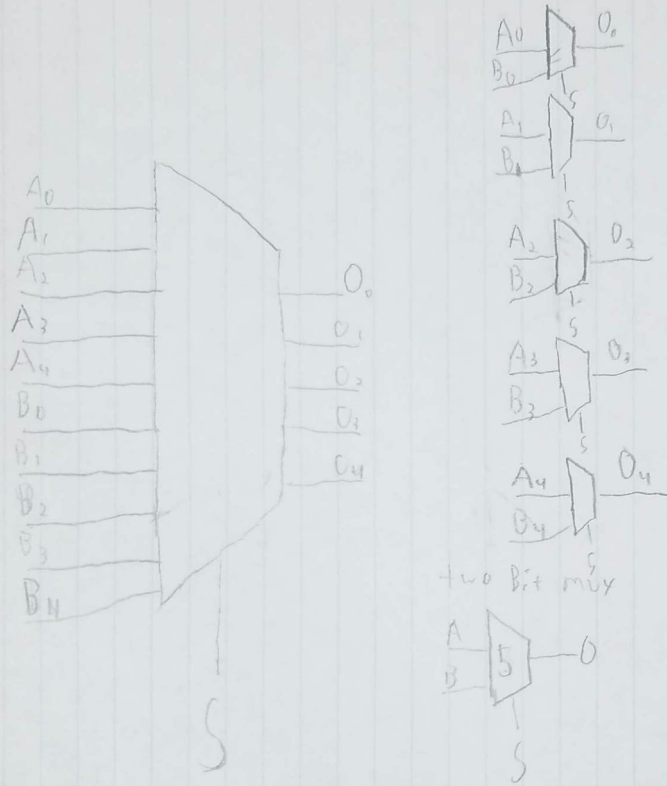This means that the Gate delay is 5, like a 2 bit mux



 

Gate delay 64 bit mux

The 64 bit mux is the same concept as the 5 bit.

Everything works in parallel, so the gate delay is 5.